

111  
429


Korhan Erdoğan 30838 ~~Korhan~~

## Lab assignment #1

- To display 7 numbers, 3 bits is enough. If we wanted to show 9 numbers we should have used 4 bits.

$d_2$	$d_1$	$d_0$	Decimal	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	1	1	0	1	1	0	0	0	0
0	1	0	2	1	1	0	1	1	0	1
0	1	1	3	1	1	1	1	0	0	1
1	0	0	4	0	1	1	0	0	1	1
1	0	1	5	1	0	1	1	0	1	1
1	1	0	6	1	0	1	1	1	1	1
1	1	1	7	1	1	1	0	0	0	0

$$a = d_2' + d_1' + d_0$$

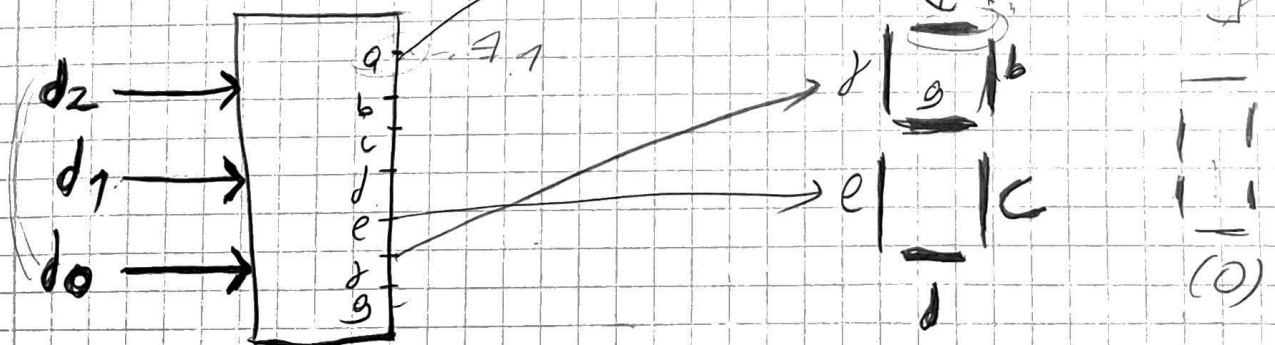

"g" means there is a line.

minterms

$$a = \sum (0, 2, 3, 5, 6, 7) = \text{minterms}$$

$$a = \underbrace{d_2' d_1' d_0'}_0 + \underbrace{d_2' d_1 d_0'}_2 + \underbrace{d_2' d_1 d_0}_3 + \underbrace{d_2 d_1' d_0'}_5 + \underbrace{d_2 d_1 d_0'}_6 + \underbrace{d_2 d_1 d_0}_7$$

$$b = \sum (0, 1, 2, 3, 4, 7)$$

$$b = \underbrace{d_2' d_1' d_0'}_0 + \underbrace{d_2' d_1' d_0}_1 + \underbrace{d_2' d_1 d_0'}_2 + \underbrace{d_2' d_1 d_0}_3 + \underbrace{d_2 d_1' d_0'}_4 + \underbrace{d_2 d_1 d_0}_7$$

$$c = \sum (0, 1, 3, 4, 5, 6, 7)$$

$$c = \underbrace{d_2' d_1' d_0'}_0 + \underbrace{d_2' d_1' d_0}_1 + \underbrace{d_2' d_1 d_0}_3 + \underbrace{d_2 d_1' d_0'}_4 + \underbrace{d_2 d_1' d_0}_5 + \underbrace{d_2 d_1 d_0'}_6 + \underbrace{d_2 d_1 d_0}_7$$

$$d = \sum (0, 2, 3, 5, 6)$$

$$d = \underbrace{d_2' d_1' d_0'}_0 + \underbrace{d_2' d_1 d_0}_2 + \underbrace{d_2' d_1 d_0'}_3 + \underbrace{d_2 d_1' d_0}_5 + \underbrace{d_2 d_1 d_0'}_6$$

$$e = \sum (0, 2, 6)$$

$$e = \underbrace{d_2' d_1' d_0'}_0 + \underbrace{d_2' d_1 d_0'}_2 + \underbrace{d_2 d_1 d_0'}_6$$


$$f = \sum (0, 4, 5, 6, 7)$$

$$f = \underbrace{d_2' d_1' d_0'}_0 + \underbrace{d_2 d_1' d_0'}_4 + \underbrace{d_2' d_1 d_0}_5 + \underbrace{d_2 d_1 d_0'}_6 + \underbrace{d_2 d_1 d_0}_7$$

$\cdot g = \{2, 3, 4, 5, 6\}$

$$g = \underbrace{d_2' d_1 d_0'}_2 + \underbrace{d_2' d_1 d_0}_3 + \underbrace{d_2 d_1' d_0'}_4 + \underbrace{d_2 d_1' d_0}_5 + \underbrace{d_2 d_1 d_0'}_6$$


Full Circuit

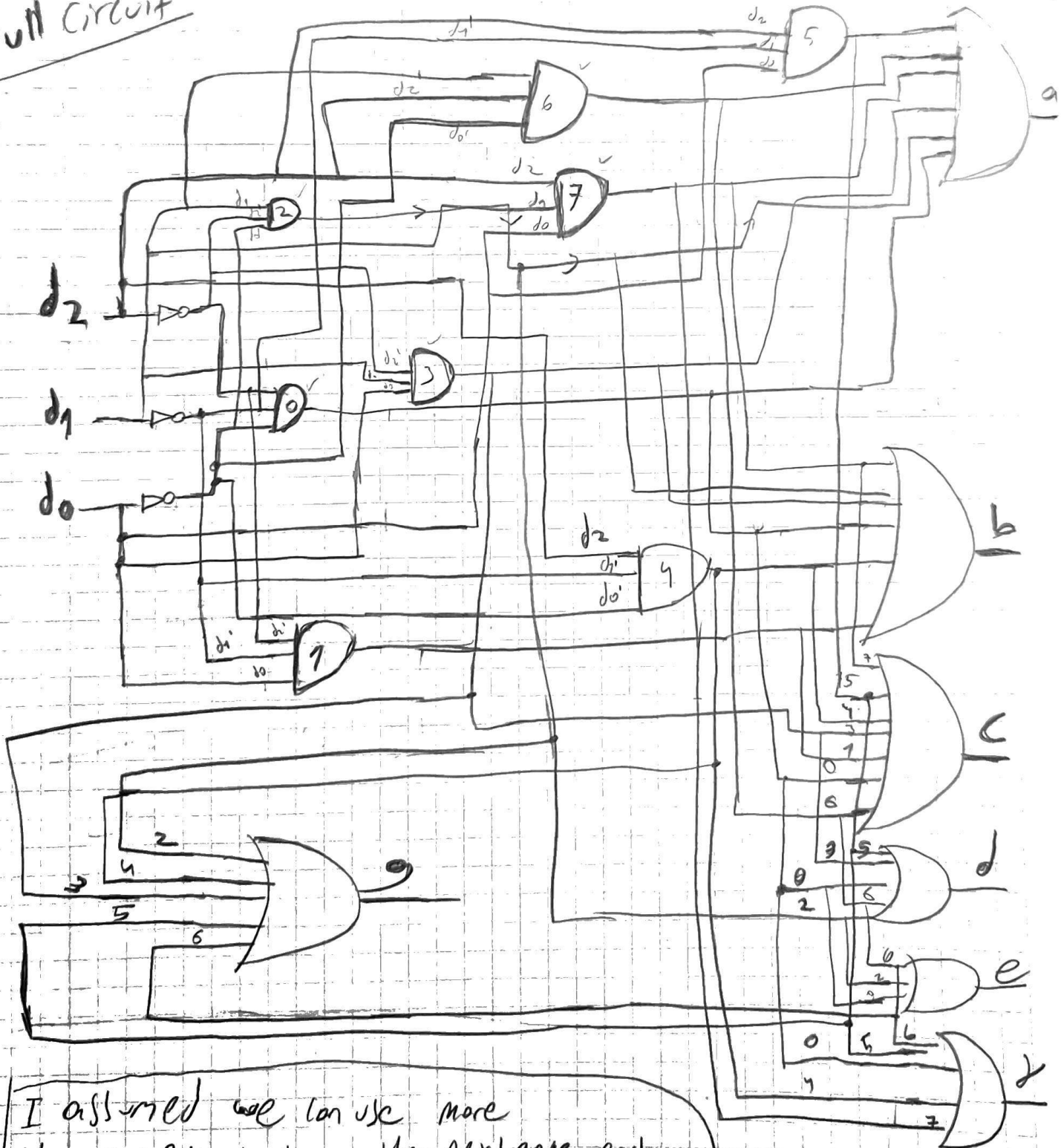

I assumed we can use more than 2 inputs but in the next page each segments are designed with 2 inputs for the gates.



2 inputs

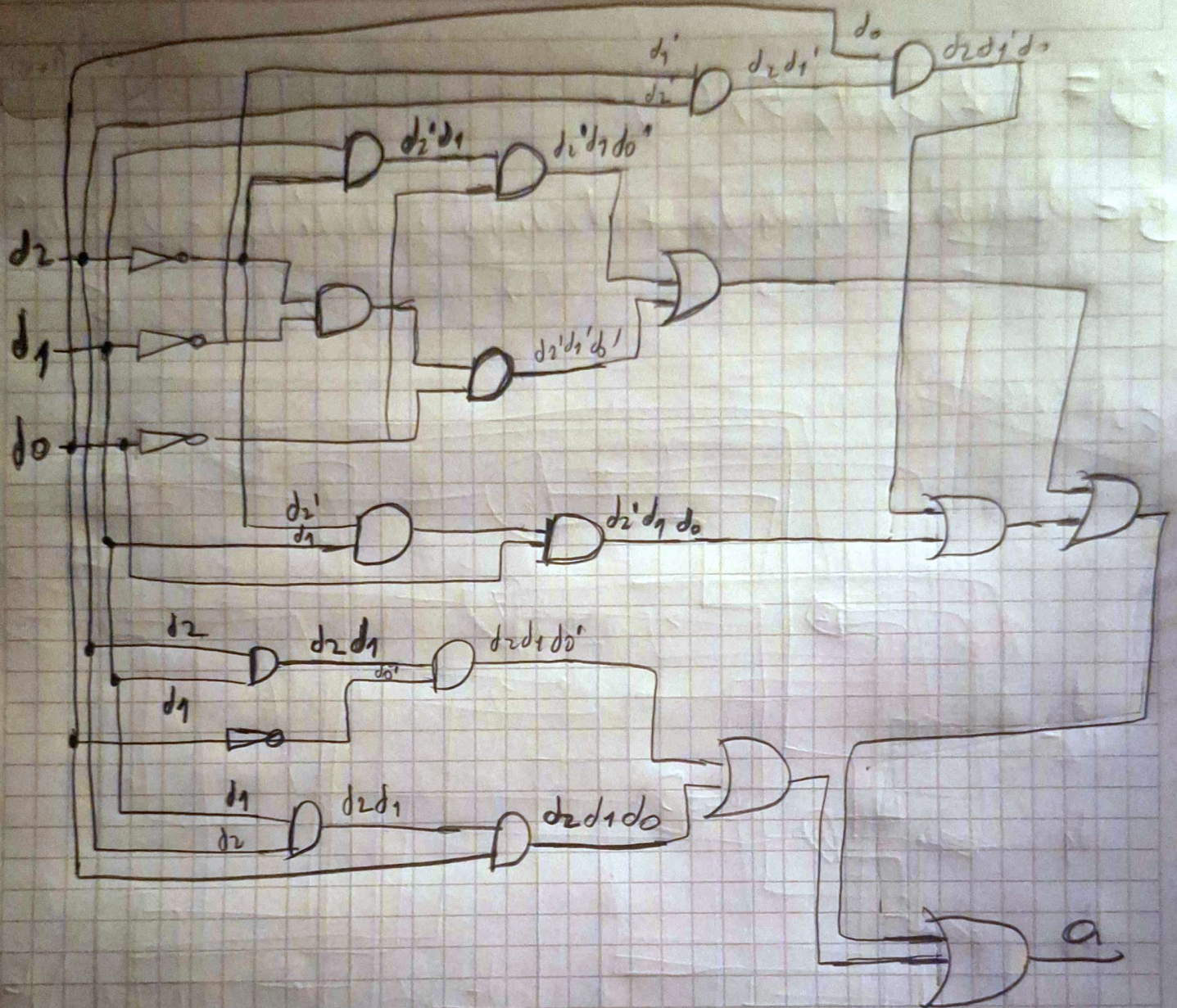

and so on...