

Distributive Law in *Digital*

Prove that addition (+) is distributive over multiplication (\cdot) by constructing two circuits to implement

- $x + yz$
- $(x + y) \cdot (x + z)$

and applying the same inputs x , y and z to the inputs of both circuits. Toggle inputs to generate all possible input combinations and observe that both circuits generate the same result.

Submit the *.dig* file you have created.

□